

EXPERIMENT-07

AIM OF THE EXPERIMENT:-

Distribution System Power factor improvement
using Switched Capacitor.

APPARATUS REQUIRED:-

- 1) High voltage Transmission line Analyzer
- 2) wattmeter : (0-600)V , (0-5-10)A - 2 Nos

LOAD SPECIFICATION:-

Resistive load : 3-ph 415V, 1.5 kW, 2A

Inductive load : 3-ph 415V, 0.75 kW, 1.9A, $\cos\phi = 0.75$

THEORY:-

Power factor is the Ratio of working power to apparent power. It measures how effectively electrical power is being used. A high Power factor signals efficient utilization of electrical power, while low Power factor indicates poor utilization of power.

$$P.f. = kW / kVA = \cos\phi, \phi = \text{angle between Voltage Current phasor}$$

It is achieved by addition of Capacitor in parallel with the connected motor or lighting circuits and can be applied at the equipment.

Caution should be taken when applying power factor correction star/delta type control so that the capacitors are not subjected to rapid on-off on condition.

OBSERVATION:-

Sl No.	Load Data R+L in KW	Load Data 'i'	Sending end voltage (in V)	Receiving end voltage (in V)	Receiving end current (in A)	Wattmeter reading (W_1)	Wattmeter reading (W_2)	P.f. (Calc)
1	1.35	0	410	191	0.53	$5 \times 8 = 40W$	$29 \times 2 = 58$	0.808
2	1.35	6-lf	410	238	0.61	$15 \times 8 = 120W$	$49 \times 2 = 98$	0.98

CALCULATION:-

$$\text{Multiplying factor for } W_1 = \frac{600 \times 5 \times 0.2}{75} = 8$$

$$\text{Multiplying factor for } W_2 = \frac{600 \times 2.5 \times 0.2}{150} = 2$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi$$

$$W_2 - W_1 = V_L I_L \sin \phi$$

$$\tan \phi = \frac{\sqrt{3} (W_2 - W_1)}{W_1 + W_2}$$


When load data 'i' = 0 lf

$$\tan \phi = \frac{\sqrt{3} (98 - 40)}{98 + 40} = 0.728$$

$$\phi = \tan^{-1} (0.728) = 0.629$$

$$\Rightarrow \cos \phi = 0.808$$

CIRCUIT DIAGRAM :-

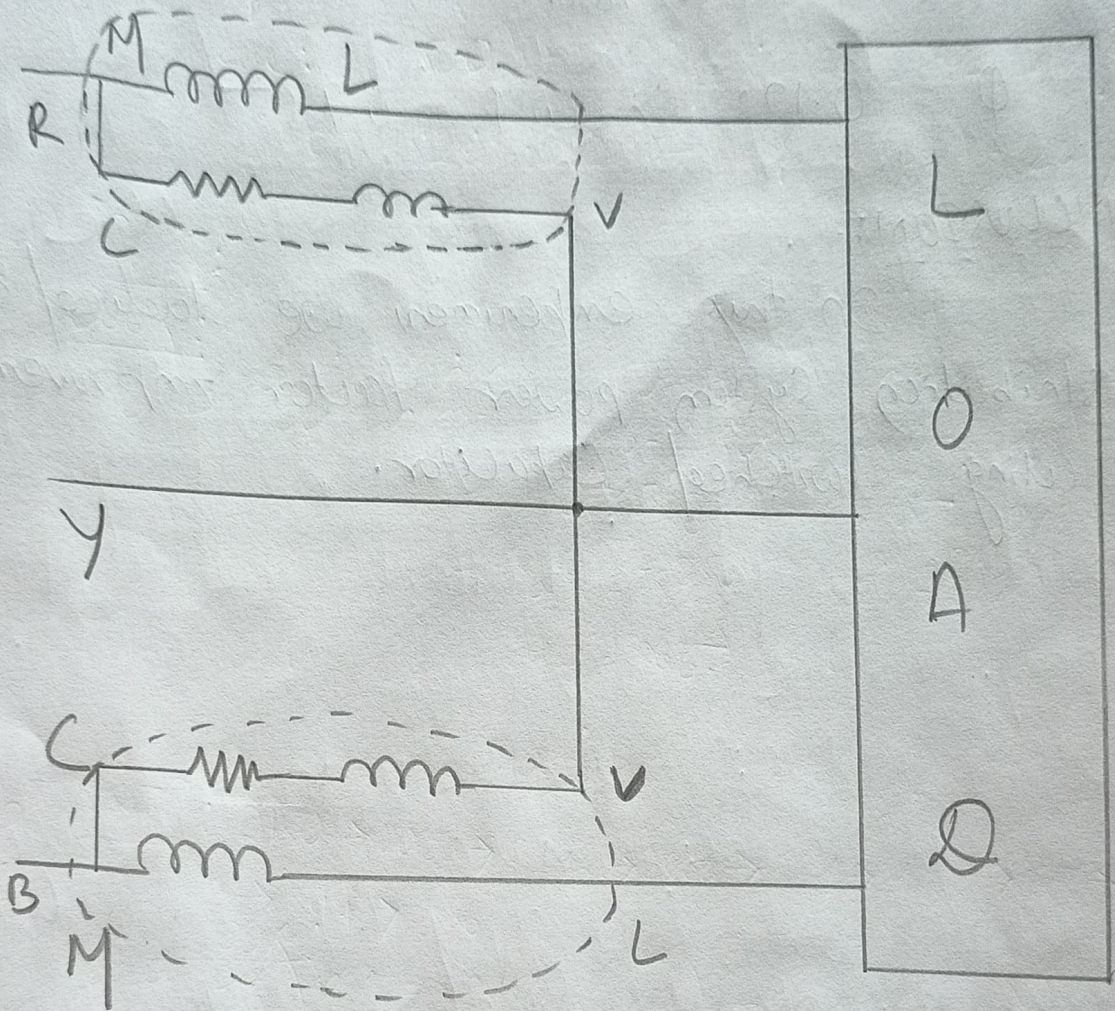

Circuit for improvement of
power factor

When load data $C = 64\mu$

$$\tan \phi = \frac{\sqrt{3} (98 - 120)}{120 + 98} = +0.1747$$

$$\phi = 0.173 \Rightarrow \cos \phi = 0.985$$

CONCLUSION:-

In this experiment, we studied about distribution system power factor improvement by using switched capacitor.

Name \rightarrow Satyabrata panda
Branch \rightarrow EEE (B₂)
SIC \rightarrow 180610185